

Set 3 BE_EXTTC May_2020, RF Design PCC-ETC801 CBCGSH

1. Maximum power transfer from the output matching network to the transistor will occur when (1M)
 - $\Gamma_L = \Gamma_{in}$
 - $\Gamma_{out} = \Gamma_s$
 - $\Gamma_{out} = \Gamma_s^*$
 - $Z_L = Z_s$

2. If $S_{11} = 0.9 \angle 180^\circ$, $S_{12} = 0.031 \angle -9^\circ$, $S_{21} = 4.250 \angle 61^\circ$, $S_{22} = 0.57 \angle -120^\circ$ for a transistor. Comment on its stability (2M)
 - Conditionally stable
 - Unconditionally stable
 - Unstable
 - oscillator


3. Find k value if $S_{11} = 0.9 \angle 180^\circ$, $S_{12} = 0.031 \angle -9^\circ$, $S_{21} = 4.250 \angle 61^\circ$, $S_{22} = 0.57 \angle -120^\circ$ (2M)
 - 0.045
 - 0.99
 - 0.383
 - 1.9

4. For the given s-parameters of a transistor calculate maximum gain $S_{11} = 0.75 \angle 180^\circ$, $S_{12} = 0$, $S_{21} = 4.50 \angle 61^\circ$, $S_{22} = 0.25 \angle -100^\circ$ (2M)
 - 16.92 dB
 - 25.1dB
 - 0.96dB
 - 1.616dB

5. A transistor having S parameters as $S_{11} = 0.6 \angle -163^\circ$, $S_{12} = 0.039 \angle 35^\circ$, $S_{21} = 7.12 \angle 86^\circ$, $S_{22} = 0.5 \angle -38^\circ$. what is centre for input stability circle (2M)
 - 1.75 \angle 171.48.
 - 1.67 \angle -48
 - 1.3 \angle -48 d.
 - 1.5 \angle 100

6. For the diagram input stability circle is drawn. If $S_{22} > 1$ then which portion of the diagram is stable region. (1M)
 - White.
 - violet
 - orange.

not inside any circle

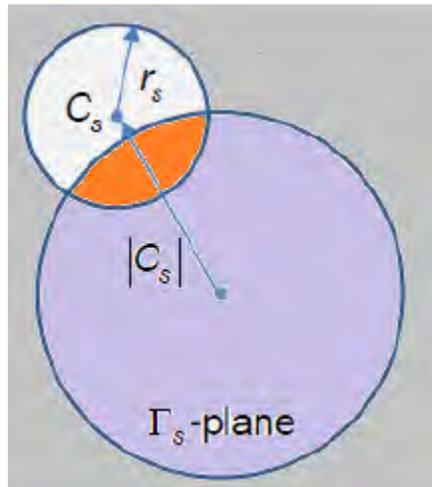

7. Major drawbacks of Constant K filter is (1M)
Slow attenuation rate after cut-off
Fast attenuation rate after cut off
Constant image impedance
Simple design
8. The Matching section of composite filter consist of (1M)
Pi sections
Bisected pi sections
T section
Bisected T section
9. For a High-pass composite filter with a cut off frequency of 4 MHz and impedance of 50ohm. There is infinite attenuation pole at 2.05 MHz. Calculate value of m (2M)
0.861
0.79
1.861
1.79
10. For a low-pass composite filter with a cutoff frequency of 2 MHz and impedance of 50ohm. There is infinite attenuation pole at 2.05 MHz. Calculate inductor value of constant k filter. (2M)
7.95 μ H
3.19 nH
8.88 μ H
3.19 μ H
11. For Chebyshev T LP filter with $g_1=2.7108$, $g_2=0.8326$, $g_3=2.7108$, $g_4=1$ and having 25MHz cut-off frequency. Calculate value of Inductor for internal impedance 75 ohm. (2M)
1.294 μ F

- 1.97 μ F
- 4.88 μ F
- 2.56 μ F

12. While designing a constant-k low pass filter (T-section) shown below, what would be the value of capacitor if $L/2 = 20\text{mH}$, $R_0 = 500 \Omega$ and $f_c = 5 \text{ kHz}$? (2M)

- 0.0635 μ F
- 0.10 μ F
- 0.1273 μ F
- 0.20 μ F

13. For a maximally flat low-pass filter with a cut off frequency of 100 GHz, impedance of 50 ohm and at least 5 dB insertion loss at 400 MHz. Calculate No of elements. (2M)

- 2
- 7
- 2
- 8

14. For 0.5dB equal-ripple pass band response if $g_1 = 1.5963$, $g_2 = 1.0967$, $g_3 = 1.5963$, $g_4 = 1.0000$ and cut-off frequency 10MHz Calculate length of the series stub (2M)

- 3.75 m
- 5 m
- 0.75 m
- 30m

15. One port oscillator uses----- at termination port (1M)

- PN junction diode
- transistor
- IMPATT diode
- resistor

16. Calculate input impedance of one port oscillator if $\Gamma_{in} = 1.75 \angle 40^\circ$ at 4GHz and $Z_0 = 50 \text{ ohm}$ (2M)

- 74.62+j81.43
- 76.153+ j84.42
- 74.62- j81.43
- 76.153+ j84.42

17. For one port oscillator design if $Z_{in} = -55.6+j102 \text{ ohm}$ what load value load impedance is required for oscillations (1M)

- 55.6+ j102
- 43.6+j122
- 43.6-j122
- 43.6- j122

18. Common-mode noise can be suppressed using ----- choke coils. (1M)

Common-mode
Differential-mode
Multimode
Transformer

19. When a common ferrite is placed on both signal and return paths, ----- noise is attenuated. (2M)
Both common mode and differential mode
Only differential mode
Only common mode
No
20. Cable to cable coupling can also be reduced by ----- over two transmission lines. (1M)
Reducing separation
Adding cable shield
Adding inductor
Adding capacitor
21. EMC ground is ----- impedance plane for voltage reference of signals. (2M)
Infinite
Zero
1 k Ω
1 M Ω
22. ----- is one of the techniques to avoid common mode impedance coupling. (1M)
Multipoint grounding
Shunt impedance
Removing ground
shorting each device with each other
23. Hybrid grounding technique works as single point ground at ----- frequency (2M)
Low
High
Medium
Both high and low
24. When individual ferrite is placed on both the signal and return paths ----- noise is suppressed. (1M)
Only differential mode
Only common mode
Both common mode and differential mode
No
25. Cable to cable coupling can also be reduced by ----- between two transmission lines. (1M)
Reducing separation
Increasing separation
Adding inductor
Adding capacitor
18. Cable to cable coupling can also be reduced by ----- both wire pairs transmission lines.
twisting

- Reducing separation between
 Adding inductor between
 Adding capacitor between (1M)
26. Protection of equipment and personnel from the hazards of lightning discharge, make -----
 very necessary. (1M)
 Bonding
 Insulation
 Use of insulated cabinet
 Use of thick insulation
27. Shield effectiveness is the ratio of -----, (2M)
 Magnitude of incident electric field to transmitted electric field
 Magnitude of incident magnetic field to transmitted electric field
 Magnitude of incident electric field to transmitted magnetic field
 Magnitude of incident electric field to transmitted power
28. A shield is good when ----- is more (1M)
 absorption loss
 Insulation
 Impedance of shield
 Its resistivity
29. Apertures on shield enclosure ----- shielding effect. (1M)
 Improves
 Reduces
 is called
 does not cause any change in
30. A desired slot in the shield is replaced by----- (1M)
 Small holes
 Transparent insulator
 Electrically opaque insulator
 A thick wooden block
31. Direct digital synthesizers utilize -----to construct an output signal waveform in the time
 domain piece by piece from a base (clock) signal. (1M)
 Comparator
 amplifier
 digital signal processing
 divider
32. Typical conversion loss numbers for a single-diode doubler are in the order of -- dB. (2M)
 10
 20
 0-5
 5-9

33. A direct frequency synthesizer offers ----- switching speed as compare to indirect frequency synthesizer. (1M)

Excellent

poor

just sufficient

lower

Set 4 BE_EXTTC May_2020, RF Design PCC-ETC801 CBCGSH

1. In a unilateral amplifier is said to be unconditionally stable if (1M)
S₁₁<1
S₁₂=0
S₂₁>1
S₁₁>1


2. A transistor having S parameters as S₁₁= 0.5∠ -100, S₁₂=0, S₂₁=5∠ 50, S₂₂=0.9∠ -60.
Comment on stability. (2M)
Conditionally stable.
Unconditionally stable.
Unstable.
partially Stable

3. For the given s-parameters of a transistor calculate k :S₁₁= 0.674∠ -152,
S₁₂=0.075∠ 6.2, S₂₁=1.74∠ 36.4, S₂₂=0.6∠ -92.6 (2M)
1.284
0.99
0.383
1.9

4. For the given s-parameters of a transistor if S₁₁= 0.65∠ -95, S₁₂=0.035∠ 40,
S₂₁=5∠ 115, S₂₂=0.8∠ -35. Determine centre of output stability circle. (2M)
1.3∠ 48.
1.67∠ -48
1.3∠ -48 d.
1.5∠ 100

5. For a transistor if S₁₁= 0.55∠ -171.3, S₁₂=0.057∠ 16.3, S₂₁=2.058∠ 28.5,
S₂₂=0.572∠ -95.7 Find Figure of merit (2M)
0.0786
0.99
0.383
1.9

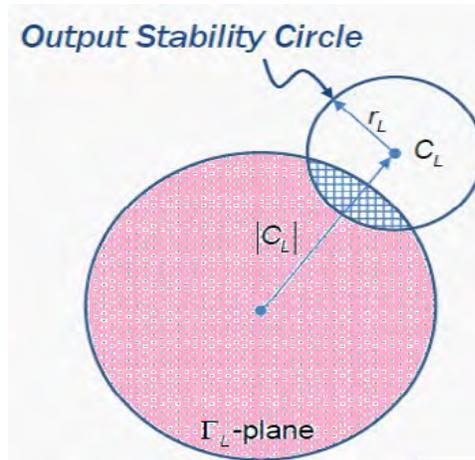6. For the diagram output stability circle is drawn. If S₁₁>1 then which portion of the
diagram is stable region. (1M)
White.
pink
blue.
not inside any circle



7. In Richards' transformation stubs can be physically separated by (1M)
 Unit element
 Series stub
 Shunt Stub
 Impedance element
8. The advantages of insertion loss methods (1M)
 Complicated design
 Shape pass and stop band of filter
 Increased loss
 Ideal response
9. For m-derived LP filter with the following specifications $R_o = 50\Omega$, $f_c = 60$ MHz and $f_\infty = 75$ MHz. Calculate value of m (2M)
 0.6
 0.79
 1.861
 1.79
10. For a constant K-filter with the following specifications $R_o = 75\Omega$, $f_c = 250$ MHz what value of inductor is required (2M)
 0.096 μ H
 16.97pH
 41.88MH
 0.056 μ H
11. For Chebyshev T filter having 1.0dB ripple with $g_1 = 1.4029$, $g_2 = 0.707$ and $g_3 = 1.9841$ and having 40MHz cut-off frequency. Calculate value of capacitor for internal impedance 50 ohm. (2M)
 159 .1pF
 160.97pF
 141.88 pF

125.56pF

12. For a low-pass filter by the image parameter method with the following specifications:
 $R_0 = 75$, $f_c = 25\text{MHz}$. What is the value of Inductor will you use? (2M)
0.955 μH
0.169 μH
4.188 μH
2.556 μH
13. For a Butterworth low-pass filter with cut-off frequency 20MHz and 30 dB insertion loss at 60 MHz Calculate No of elements. (2M)
3
5
2
6
14. For 1dB equal-ripple pass band response if $g_1 = 2.0237$, $g_2 = 0.9941$, $g_3 = 2.0237$, $g_4 = 1.000$. Calculate, impedance of shunt stub for T filter. (2M)
1.005 ohm
2.0237 ohm
0.9941ohm
1.0237 ohm
15. Negative resistance implies (2M)
 $\Gamma_{in}=1$
 $\Gamma_{in}=0$
 $\Gamma_{in}<1$
 $\Gamma_{in}>1$
16. Calculate input impedance of one port oscillator if $\Gamma_{in}=1.5 \angle 40$ at 4GHz and $Z_0=50$ ohm (2M)
 $-65.65 + j101.28$
 $67 + j122$
 $2.63 + j122$
 $5.414 + j101.28$.
17. For one port oscillator design if $\Gamma_{in} = 1.45 \angle 50$ calculate Z_{in} required for oscillations if $Z_0=100$ ohm (2M)
 $-89.02 + j179.38$
 $89.02 - j179.38$
 $93.6 - j122$
 $-93.6 - j122$
18. Common mode impedance coupling interference can also be mitigated by ----- (1M)
Shunt impedance
Single point grounding

Removing ground
shorting each device with each other

19. ----- technique has single and multi-point grounds. (1M)
Hybrid grounding
Multipoint grounding
High and low grounding
High frequency grounding
20. Hybrid grounding technique works as multi point ground at ----- frequency (2M)
Low
High
Medium
Both high and low
21. The interference due to coupling between source and victim separated without any wired connection is called----- (1M)
Source Victimization
Radiated EMI
Conducted EMI
load Victimization
22. If cables and signal transmission lines are poorly ----- then radiated EMI occurs. (2M)
Installed
Shielded
Manufactured
Separated
23. ----- coupling of EM energy leads to radiated EMI. (1M)
Capacitive
Resistive
Conducted
Source-victim
24. A ----- choke coil is used to suppress common-mode noise. (1M)
Common-mode
Differential-mode
Multimode
Transformer
25. ----- noise can be attenuated with the help of a common ferrite placed on both signal and return paths. (2 M)
Both common mode and differential mode
Only differential mode
Only common mode
No

26. ----- over two transmission lines can also be used to reduce cable to cable coupling.(1M)
- Reducing separation
 - Adding cable shield
 - Adding inductor
 - Adding capacitor
27. Accumulation of static charges can be prevented with the help of ----- . (1M)
- Highly insulated cabinet
 - Bonding
 - A thick insulator
 - Thin Insulated cover for entire circuit
28. A shield is good when ----- is more (1M)
- Reflection loss
 - Insulation
 - Impedance of shield
 - Its resistivity
29. Shielding is compromised due to intentional----- (1M)
- Low impedance
 - Ventilation and slots
 - High insulated coating
 - Inclusion of high resistive coating
30. A slot in the direction of ----- has much less effect on the shielding (1M)
- Current
 - Voltage
 - Power
 - Radiated field
31. Small holes replacing slot in a shield behave like ----- . (1M)
- Transmission path
 - Waveguide
 - Cooling medium
 - high impedance current path
18. The elementary dividers are ----- to obtain higher division coefficients in frequency divider in frequency synthesizer. (1M)
- Cascaded
 - Cascaded
 - D-F/F
 - T-F/F
29. A ----- component is used as multiplier in a frequency synthesizer. (1M)
- Low pass filter
 - band pass filter
 - nonlinear
 - linear
31. ----- switching speed is achieved in a direct frequency synthesizer as compare to indirect frequency synthesizer. (1M)

Excellent
poor
just sufficient
lower