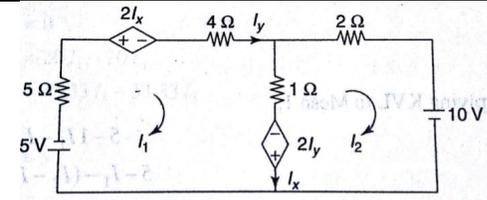
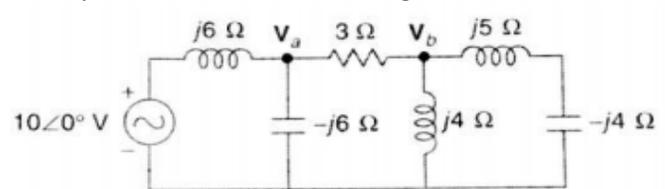
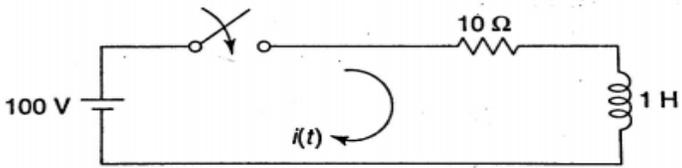


SAMPLE PAPER
ESE KT
SE (ELEX)/CBCGS-H-SEM-III
Electrical Networks

Q. No.	Objective Questions
1	If the current of source depends upon some other current in the network, it is called as – a. Independent source b. Current dependent source c. Uncontrolled source d. Variable source
2	Node is a junction where ----- network element are connected together. a. Two or more b. Only one c. Resistance d. Only two
3	Superposition Theorem is applicable to – a. Non-linear elements b. Dependent voltage source c. Dependent current source d. Linear elements
4	If the value of Current Source in the circuit is depending on some other current source present in the network, then it is called as – a. VCVS b. VCCS c. CCVS d. CCCS
5	According to Millman's Theorem, if there are n voltage sources with n internal resistances respectively, are in parallel, then these sources are replaced by? a. single current source I' in series with R' b. single voltage source V' in series with R' c. single current source I' in parallel to R' d. single voltage source V' in parallel to R'
6	In A.C. circuits the Cramer's rule is to solved – a. Complex matrix b. Simple matrix c. Identity matrix d. Diagonal matrix
7	When Inductance's are in Parallel, the differential coupling is – a. $L_{Differential} = \frac{L_1 L_2 + M^2}{L_1 + L_2 + 2M}$ b. $L_{Differential} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$

	<p>c. $L_{Differential} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$</p> <p>d. $L_{Differential} = \frac{L_1 L_2 - M^2}{L_1 - L_2 + 2M}$</p>
8	<p>When energy transfer takes place from one circuit to the other without having any electrical connections between them –</p> <ol style="list-style-type: none"> Two circuits are said to parallel circuits Two circuits are said to coupled circuits Two circuits are said to series circuits Two circuits are said to simple circuits
9	<p>The coefficient of self-inductance is represented by –</p> <ol style="list-style-type: none"> L R C R-C
10	<p>In transient analysis of electrical network arbitrary constants are determine by using –</p> <ol style="list-style-type: none"> Final conditions Initial conditions Normal conditions Steady state conditions
Short Questions	
11	<p>The equivalent circuit of capacitor at t = infinity is represented as --</p> <ol style="list-style-type: none"> Short circuit Open circuit Resistance Inductance
12	<p>The equivalent circuit of inductance with caring current (I₀), at t = 0+ is represented as –</p> <ol style="list-style-type: none"> Current source of I₀ Voltage source of V₀ Voltage source of V₀ with parallel O.C. Voltage source of V₀ with parallel S.C.
13	<p>The equivalent circuit of inductor at t = infinity is represented as --</p> <ol style="list-style-type: none"> Short Circuit Open circuit Resistance Inductance
14	<p>Identify the correct equation for mesh 1.</p>

	<div style="text-align: center;">  </div> <p>a. $KVL_1 = -5 - 5I_1 - 2I_x - 4I_1 - 1(I_1 - I_2) + 2I_y = 0$ b. $KVL_1 = -5 - 5I_1 - 2I_x - 4I_1 - 1(I_1 + I_2) + 2I_y = 0$ c. $KVL_1 = +5 + 5I_1 - 2I_x - 4I_1 - 1(I_1 - I_2) + 2I_y = 0$ d. $KVL_1 = -5 - 5I_1 + 2I_x + 4I_1 - 1(I_1 - I_2) + 2I_y = 0$</p>
15	<p>The conditions existing just after switching are represented by –</p> <p>a. $i(0^+), v(0^-)$ b. $i(0^-), v(0^+)$ c. $i(0^-), v(0^-)$ d. $i(0^+), v(0^+)$</p>
16	<p>Identify the KCL at nodal V_b for a given network –</p> <div style="text-align: center;">  </div> <p>a. $\frac{V_b - V_a}{3} + \frac{V_b}{j4} + \frac{V_b}{j1} = 0$ b. $\frac{V_b + V_a}{3} + \frac{V_b}{j4} + \frac{V_b}{j1} = 0$ c. $\frac{V_b - V_a}{3} + \frac{V_b}{j4} - \frac{V_b}{j1} = 0$ d. $\frac{V_b - V_a}{3} - \frac{V_b}{j4} + \frac{V_b}{j1} = 0$</p>
17	<p>For thevenins theorem steps are mentioned arrange in correct order –</p> <ol style="list-style-type: none"> 1. Remove the load resistance R_L 2. Find the resistance R_{th} as seen from point A and B. 3. Find the open circuit voltage V_{th} across points A and B. 4. Find the current through R_L using Ohm's law. 5. Replace the network by a voltage source V_{th} in series with resistance R_{th}

	<p>a. 1, 3, 2, 5, 4 b. 1, 2, 4, 3, 5 c. 1, 4, 3, 5, 2 d. 1, 5, 4, 3, 2</p>
18	<p>For the network shown find the value of current at $t = 0^+$</p>  <p>a. Current $i(0)$ at $t = 0^+$ is 10 b. Current $i(0)$ at $t = 0^+$ is 1 c. Current $i(0)$ at $t = 0^+$ is 0 d. Current $i(0)$ at $t = 0^+$ is 11</p>
19	<p>Find the value of V_1 for the matrix shown.</p> $\begin{bmatrix} 0.62 - j0.16 & -0.5 \\ -0.5 & 0.5 - j0.3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \angle 0^\circ \\ 0 \end{bmatrix}$ <p>a. $V_1 = 21.8 \angle 56.42^\circ$ b. $V_1 = 31.8 \angle 56.42^\circ$ c. $V_1 = 41.8 \angle 56.42^\circ$ d. $V_1 = 51.8 \angle 56.42^\circ$</p>
20	<p>For a two port network to be Symmetrical –</p> <p>a. $Z_{11} Z_{22} - Z_{12} Z_{21} = 1$ b. $AD - BC = 1$ c. $h_{11} h_{22} - h_{12} h_{21} = 1$ d. $Y_{11} Y_{22} - Y_{12} Y_{21} = 1$</p>