

- 9. The condition for non conducting mode is** [1]
a) V_{ds} lesser than V_{gs} b) V_{gs} lesser than V_{ds}
c) $V_{gs} = V_{ds} = 0$ d) $V_{gs} = V_{ds} = V_s = 0$
- 10. nMOS is** [1]
a) donor doped b) acceptor doped
c) all of the mentioned d) none of the mentioned
- 11. MOS transistor structure is** [1]
a) symmetrical b) non symmetrical
c) semi symmetrical d) pseudo symmetrical
- 12. As source drain voltage increases, channel depth** [1]
a) increases b) decreases
c) logarithmically increases d) exponentially increases
- 13. If p-transistor is conducting and has small voltage between source and drain, then the it is said to work in** [1]
a) linear region b) saturation region
c) non saturation resistive region d) cut-off region
- 14. Mobility depends on** [1]
a) transverse electric field b) V_g
c) V_{dd} d) Channel length
- 15. NOR type flash allows _____ to be read or written independently** [1]
a) one machine cycle b) one machine word
c) one machine sentence d) one bit
- 16. NAND type flash memories are used in** [1]
a) memory cards b) USB
c) solid state drivers d) all of the mentioned
- 17. The transistors in NAND type flash are connected in** [1]
a) series b) parallel c) cascade d) randomly
- 18. The program erase cycle in flash memory is** [1]
a) finite b) infinite c) all of the mentioned d) none of the mentioned

- 19. In Pseudo-nMOS logic, n transistor operates in** [1]
- a) cut off region
 - b) saturation region
 - c) resistive region
 - d) non saturation region
- 20. The power dissipation in Pseudo-nMOS is reduced to about _____ compared to nMOS device.** [1]
- a) 50%
 - b) 30%
 - c) 60%
 - d) 70%
- 21. Pseudo-nMOS has higher pull-up resistance than nMOS device.** [1]
- a) true
 - b) false
- 22. In dynamic CMOS logic _____ is used.** [1]
- a) two phase clock
 - b) three phase clock
 - c) one phase clock
 - d) four phase clock
- 23. In clocked CMOS logic, output is evaluated in** [1]
- a) on period
 - b) off period
 - c) both periods
 - d) half of on period
- 24. In clocked CMOS logic, rise time and fall time are** [1]
- a) faster
 - b) slower
 - c) faster first and then slows down
 - d) slower first and then speeds up
- 25. Clocked sequential circuits are** [1]
- a) two phase overlapping clock
 - b) two phase non overlapping clock
 - c) four phase overlapping clock
 - d) four phase non overlapping clock

26. When both nMOS and pMOS transistors of CMOS logic gates are ON, the output is:

[1]

- a) 1 or V_{DD} or HIGH state
- b) 0 or ground or LOW state
- c) Crowbarred or Contention(X)
- d) Less than V_{DD}

27. For carry skip adder, the minimum total propagation delay can be obtained when m is

[1]

- a) $\sqrt{nk_1/k_2}$
- b) $\sqrt{2nk_1/k_2}$
- c) $\sqrt{2k_1/nk_2}$
- d) $\sqrt{nk_1k_2/2}$

28. Multiple output domino logic has

[1]

- a) two cell manchester carry chain
- b) three cell manchester carry chain
- c) four cell manchester carry chain
- d) four cell manchester carry look ahead

29. Which method uses reduced number of partial products?

[1]

- a) Baugh-wooley algorithm
- b) Wallace trees
- c) Dadda multipliers
- d) Modified booth encoding


30. Which method is easier to manipulate accumulator content?

[1]


- a) left shifting
- b) right shifting
- c) serial shifting
- d) parallel shifting

31. The CMOS logic circuit for NAND gate is:


[2]

 


a.

 

b.

 

c.

 

d.

32. What type of logic gate's behaviour does this truth table represent? [2]

?			
A	B	C	?
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

- a. 2 input OR b. 3 input OR c. 3 input EXOR d. 4 input EXOR


33. How many bits must each word have in one-to-four line de-multiplexer to be implemented using a memory? [2]

- a) 8 bit b) 4 bits c) 2 bits d) 1 bits

34. A full Adder has.... [2]

- a) 2 inputs, 2 outputs
b) 2 inputs, 1 output
c) 3 inputs, 2 outputs
d) 3 inputs, 1 output

 35. Determine the Noise Margin for 5V TTL inverter gate: [2]



- a) NMH = 0.4V and NML = 0.4V
b) NMH = 2.4V and NML = 0.4V
c) NMH = 2V and NML = 0.8V
d) NMH = 1.5V and NML = 0.4V

36. The switching threshold voltage V_{TH} for an ideal inverter is equal to: [2]

- a) $(V_{DD}-V_{OL})/2$
- b) V_{DD}
- c) $(V_{DD})/2$
- d) 0

37. In VLSI design, which process deals with the determination of resistance & capacitance of interconnections? [2]

- a. Floorplanning
- b. Placement & Routing
- c. Testing
- d. Extraction

38. The output of sequential circuit is regarded as a function of time sequence of _____. [2]

A. Inputs B. Outputs C. Internal States D. External States

- a. A & D
- b. A & C
- c. B & D
- d. B & C

39. Which method/s of physical clocking is/are a /the recursive structure where the memory elements are grouped together to make the use of nearby or same distribution points? [2]

- a. H tree
- b. Balanced tree clock network
- c. Random Tree
- d. I tree

40. For a pseudo nMOS design the impedance of pull up and pull down ratio is [2]

- a) 4:1
- b) 1:4
- c) 3:1
- d) 1:3

Note: These Questions are only for display purpose